

Shifters & Multipliers


Amin Rezaei

CECS 361 - Digital Design Techniques and Verification

California State University, Long Beach


Linear Shifter

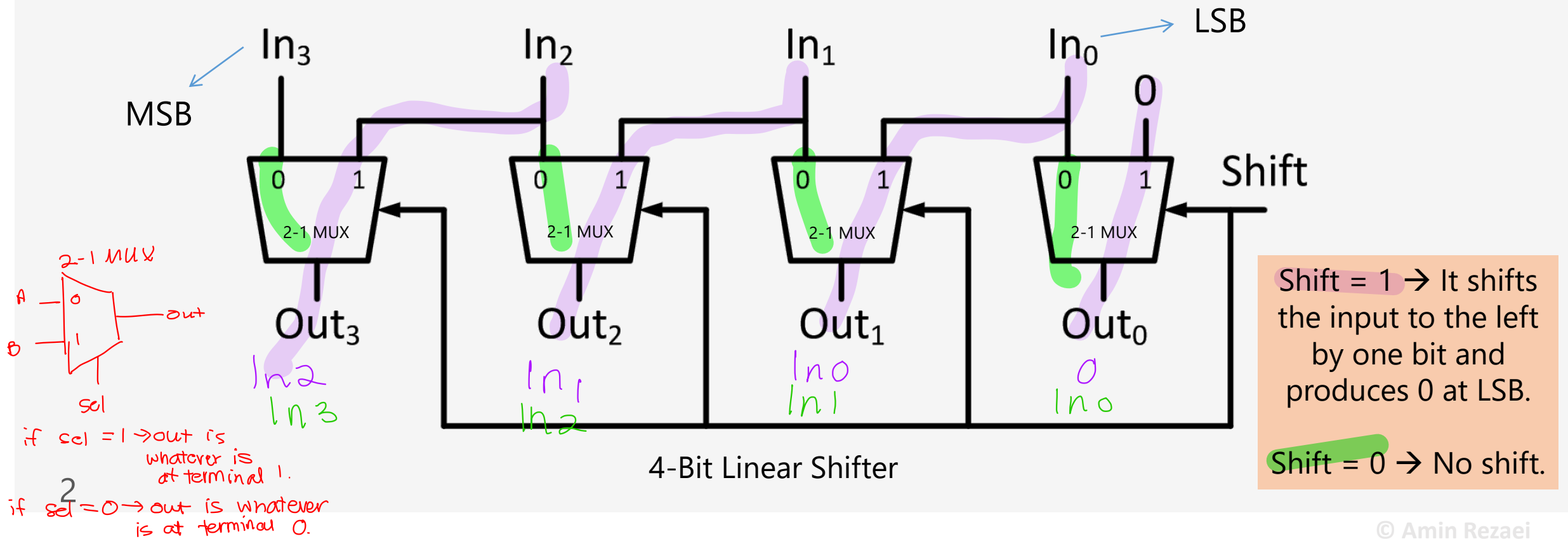Linear shifter shifts its inputs by a number of bits to the right or to the left, and routes the result to its output.




Barrel Shifter

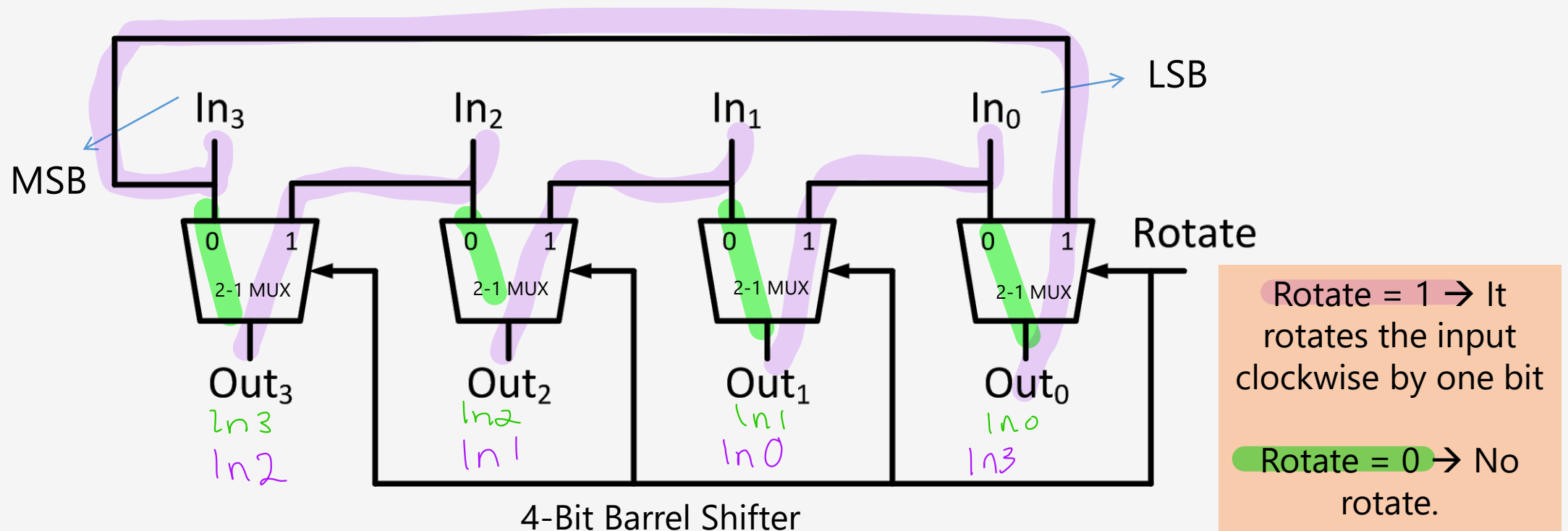Barrel shifter rotates its inputs in either clockwise or counterclockwise direction by a number of bits and propagate them to their outputs.



Shifter - Sample Question

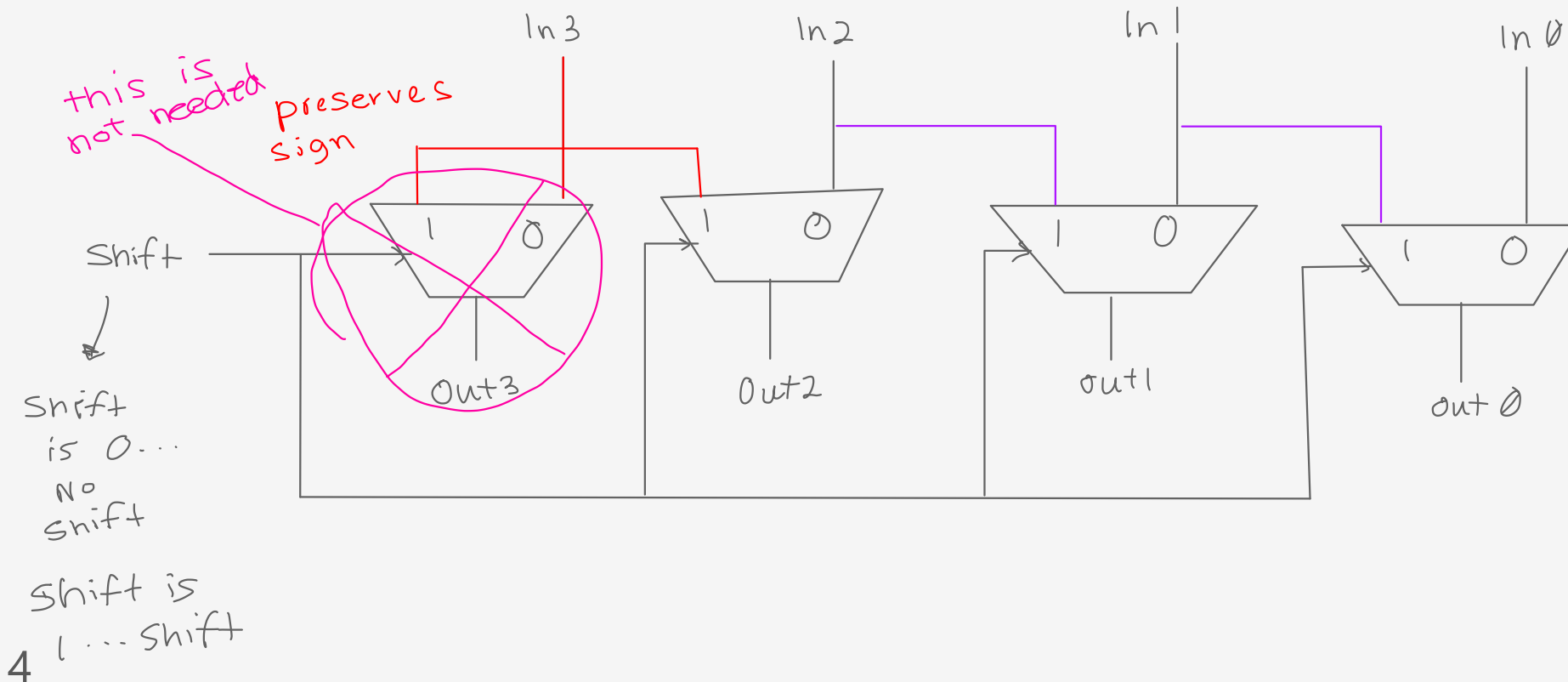
Design a 4-bit arithmetic linear shifter that shifts its inputs to the right by one bit and keep the sign bit.



Shifter - Sample Question - Solution

Divider by 2.

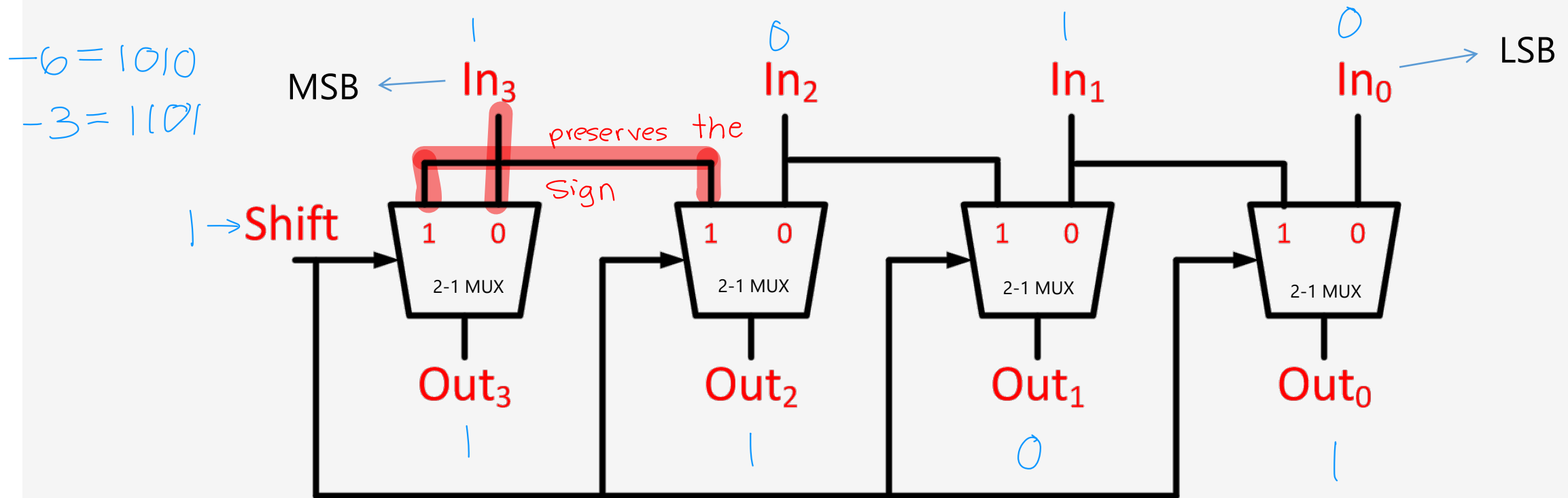Design a 4-bit arithmetic linear shifter that shifts its inputs to the right by one bit and keep the sign bit.



Array Multiplier

Array multiplier generates all partial products before summing each column in the partial product tree to obtain the result.

				A ₃	A ₂	A ₁	A ₀	Multiplicand
				B ₃	B ₂	B ₁	B ₀	Multiplier
			X					
				B ₀ .A ₃	B ₀ .A ₂	B ₀ .A ₁	B ₀ .A ₀	Partial Product 0 th
			B ₁ .A ₃	B ₁ .A ₂	B ₁ .A ₁	B ₁ .A ₀		Partial Product 1 th
		B ₂ .A ₃	B ₂ .A ₂	B ₂ .A ₁	B ₂ .A ₀			Partial Product 2 nd
	B ₃ .A ₃	B ₃ .A ₂	B ₃ .A ₁	B ₃ .A ₀				Partial Product 3 rd
+								
Sum ₇	Sum ₆	Sum ₅	Sum ₄	Sum ₃	Sum ₂	Sum ₁	Sum ₀	Sum Output

Array Multiplier - Sample Question 1

Unsigned

Multiply 13 and 9 according to the rules of array multiplication.

$$13 = (1101)_2$$

$$a = (1001)_2$$

$$13(a) = 117 = (1110101)_2$$

[illegible]

$$64 + 32 + 16 + 4 + 1$$

Handwritten calculation showing the sum of powers of 2:

$$\begin{array}{r} \underbrace{64 + 32}_{96} + \underbrace{16 + 4}_{20} + 1 \\ \quad \quad \quad \underbrace{\qquad\qquad\qquad}_{21} \\ \qquad\qquad\qquad \underbrace{\qquad\qquad\qquad}_{117} \end{array}$$

Array Multiplier - Sample Question 1 - Solution

Multiply 13 and 9 according to the rules of array multiplication.

13 = (1101)_b

9 = (1001)_b

				1	1	0	1	Multiplicand
				1	0	0	1	Multiplier
				x				
				1	1	0	1	Partial Product 0 th
			0	0	0	0		Partial Product 1 th
		0	0	0	0			Partial Product 2 nd
	1	1	0	1				Partial Product 3 rd
				+				
	0	1	1	1	0	1	0	1
								Sum Output

(01110101)_b = 117

Array Multiplier - Sample Question 2


Design the partial product tree for 4-bit array multiplier.

				A_3	A_2	A_1	A_0	Multiplicand
				B_3	B_2	B_1	B_0	Multiplier
				X				
				$B_0.A_3$	$B_0.A_2$	$B_0.A_1$	$B_0.A_0$	Partial Product 0 th
				$B_1.A_3$	$B_1.A_2$	$B_1.A_1$	$B_1.A_0$	Partial Product 1 th
				$B_2.A_3$	$B_2.A_2$	$B_2.A_1$	$B_2.A_0$	Partial Product 2 nd
				$B_3.A_3$	$B_3.A_2$	$B_3.A_1$	$B_3.A_0$	Partial Product 3 rd
+								
Sum ₇	Sum ₆	Sum ₅	Sum ₄	Sum ₃	Sum ₂	Sum ₁	Sum ₀	Sum Output

Array Multiplier - Sample Question 2 - Solution


Design the partial product tree for 4-bit array multiplier.

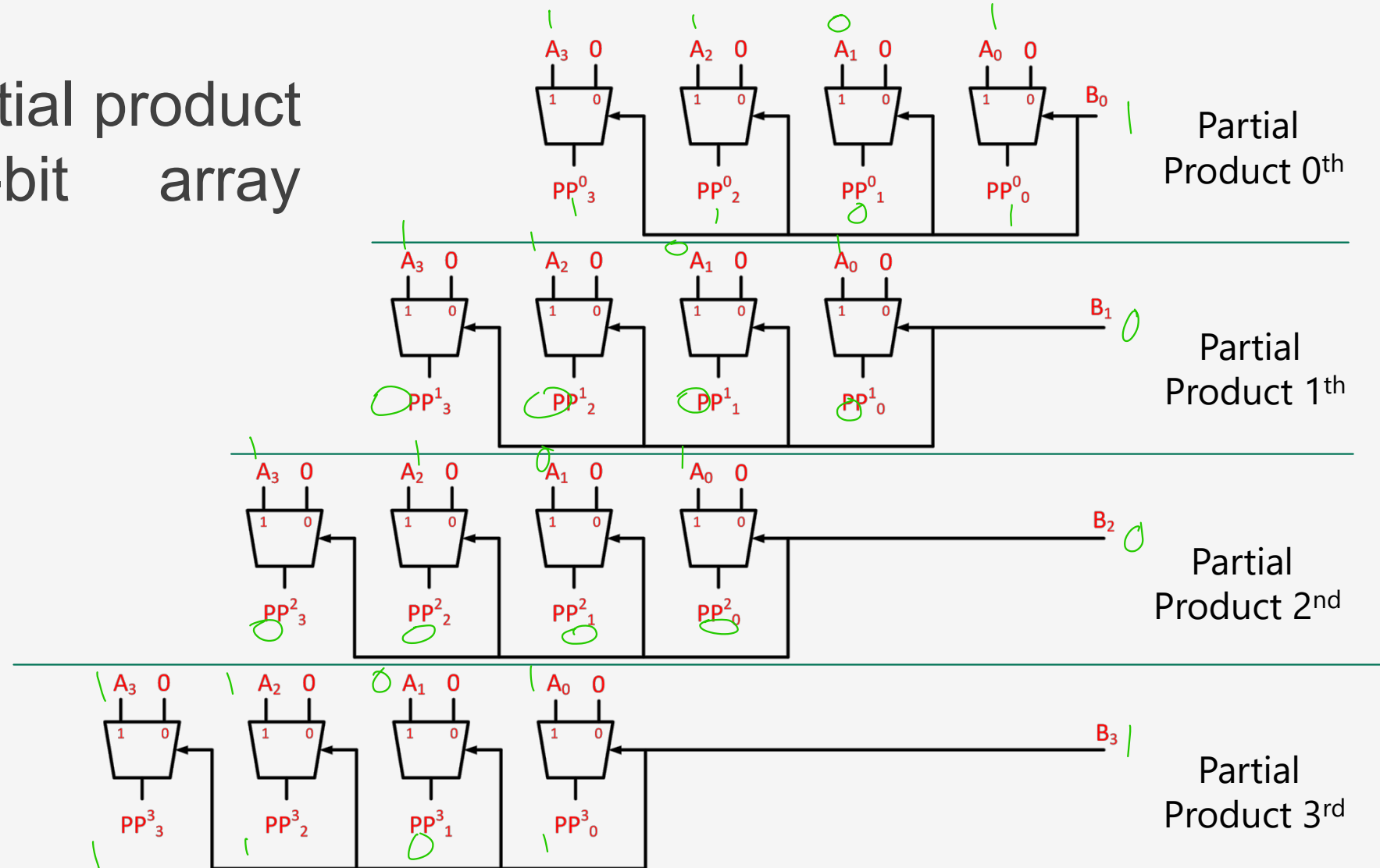$\text{PP}_{\#}^{\#}$ row/upper index
position




Array Multiplier - Sample Question 3

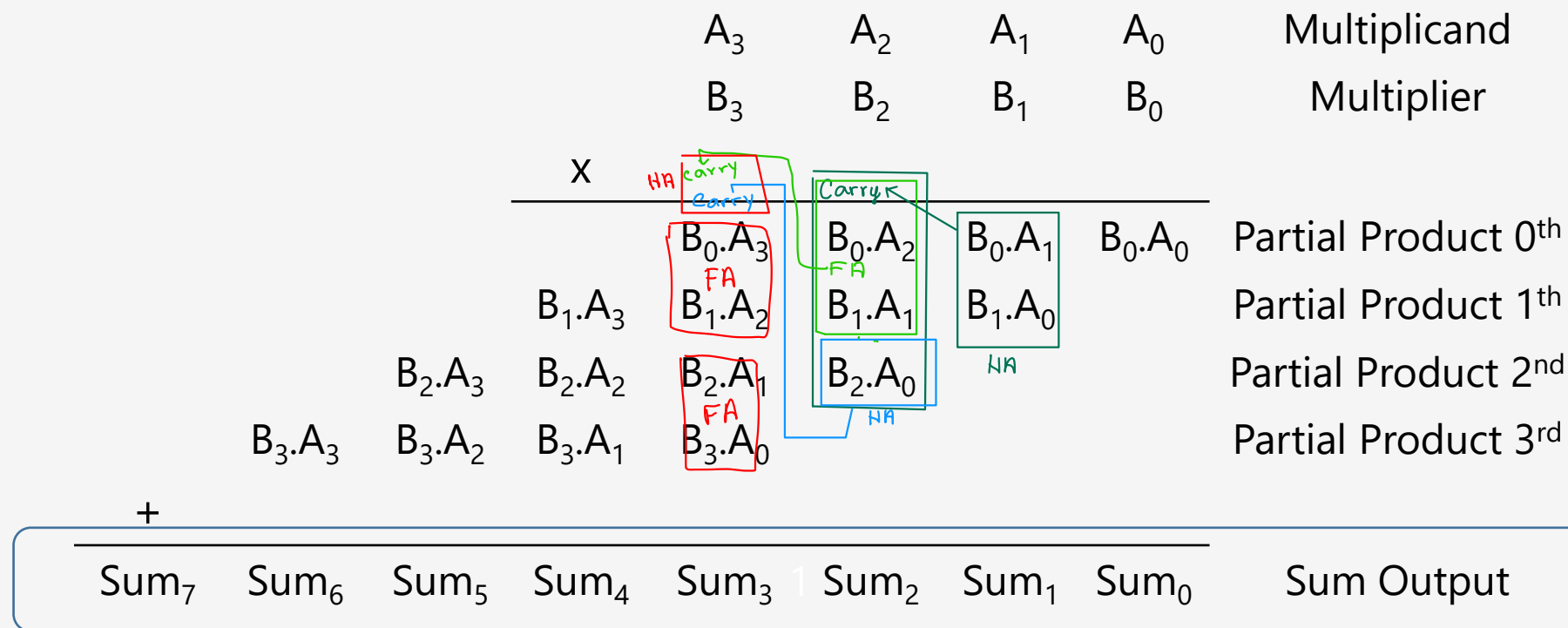Design full adder tree responsible for adding every partial product in the partial product tree for 4-bit array multiplier.



Array Multiplier - Sample Question 3 - Solution

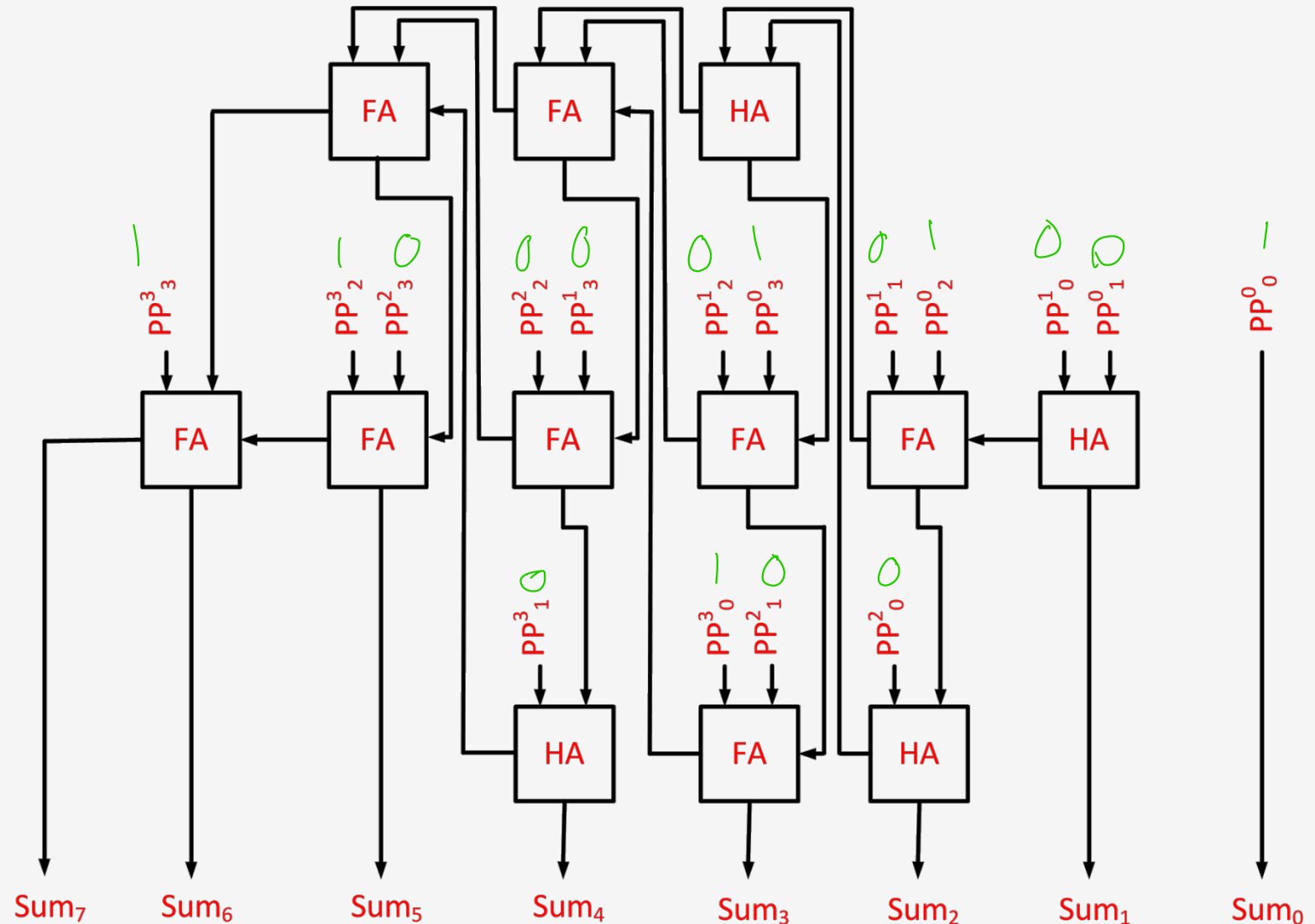Design full adder tree responsible for adding every partial product in the partial product tree for 4-bit array multiplier.



Homework Assignment 1

Due Date: Check Canvas. Sep 16.

Late Submission Policy:

One day delay: 25% deduction

Two days delay: 50% deduction

More than two days delay: No credit

Academic Integrity: There is zero tolerance for cheating, plagiarism, or any other act of violation of Academic Integrity.